Mirror

Moonn Electronics

Use me to build a version of the Tripple Fuzz by Tim Escobedo

Hi there!
Thank you for building me!

Obscure fuzz is good fuzz!

If you have any questions or anything else to say, just write an email to
moonnelectronics@gmail.com

Have a nice day!

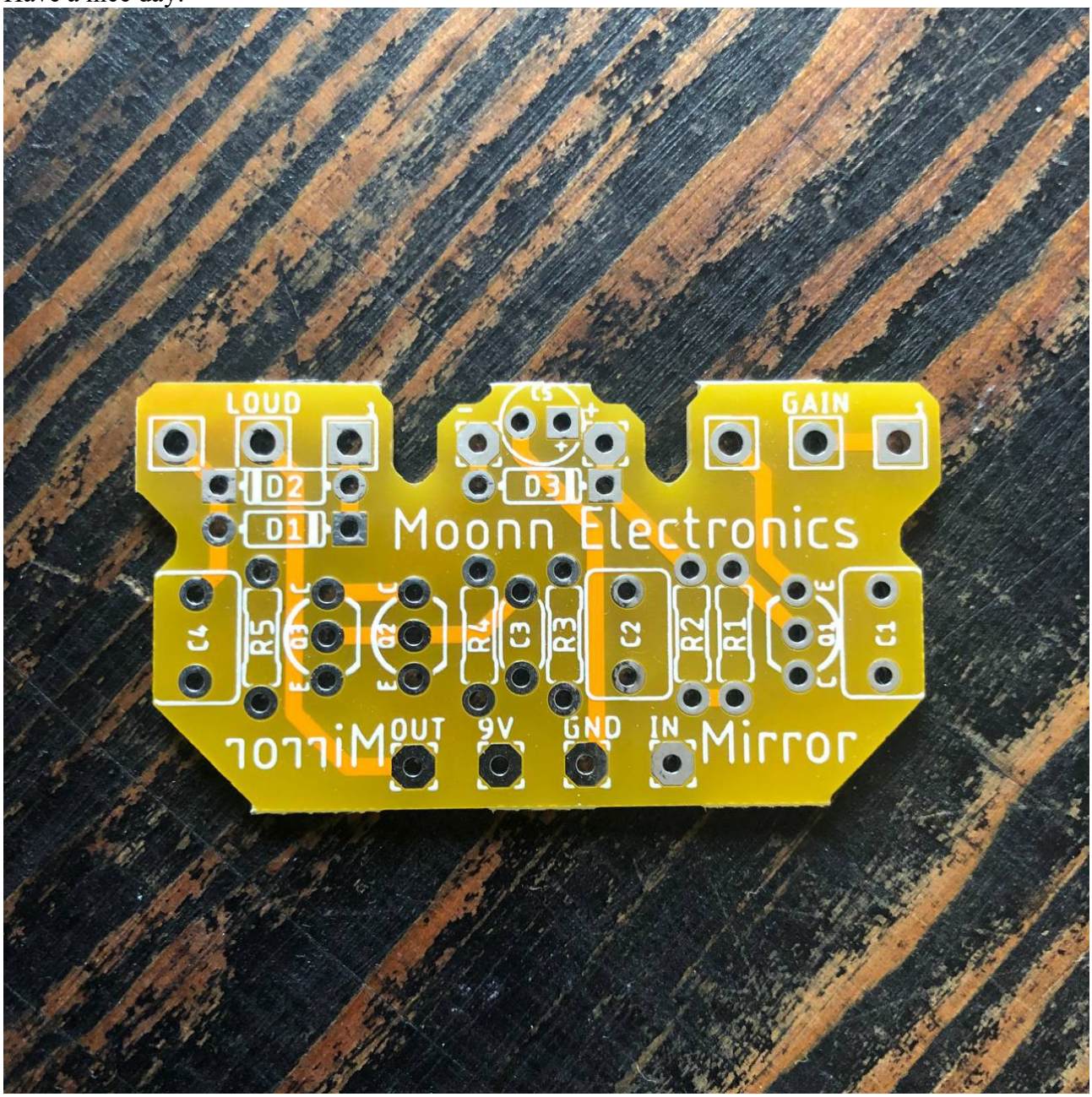

Moonn Electronics is in no way affiliated with Tim Escobedo

Bill of Materials

Qty	Value	Parts	
Resistors			
3	10K	R2, R4, R5	
1	500K	R3	
1	4M7	R1	
Film and Ceramic Capacitors			
1	220p	C3**	
3	1u	C1*, C2, C4*	
Electrolytic Capacitors			
1	100u	C5	
Semiconductors			
2	1N4148	D1, D2	Try any silicon diodes
1	1N4001	D3	
1	MPSA18	Q1	
1	2N3906	Q2	
1	2N3904	Q3	
Switches and Potentiometers			
1	A100K	LOUD	
1	B100K	GAIN	

*The original schematic has 100n in these positions but I think its nicer like this

**You might wanna try to increase the value for more bass

Schematic

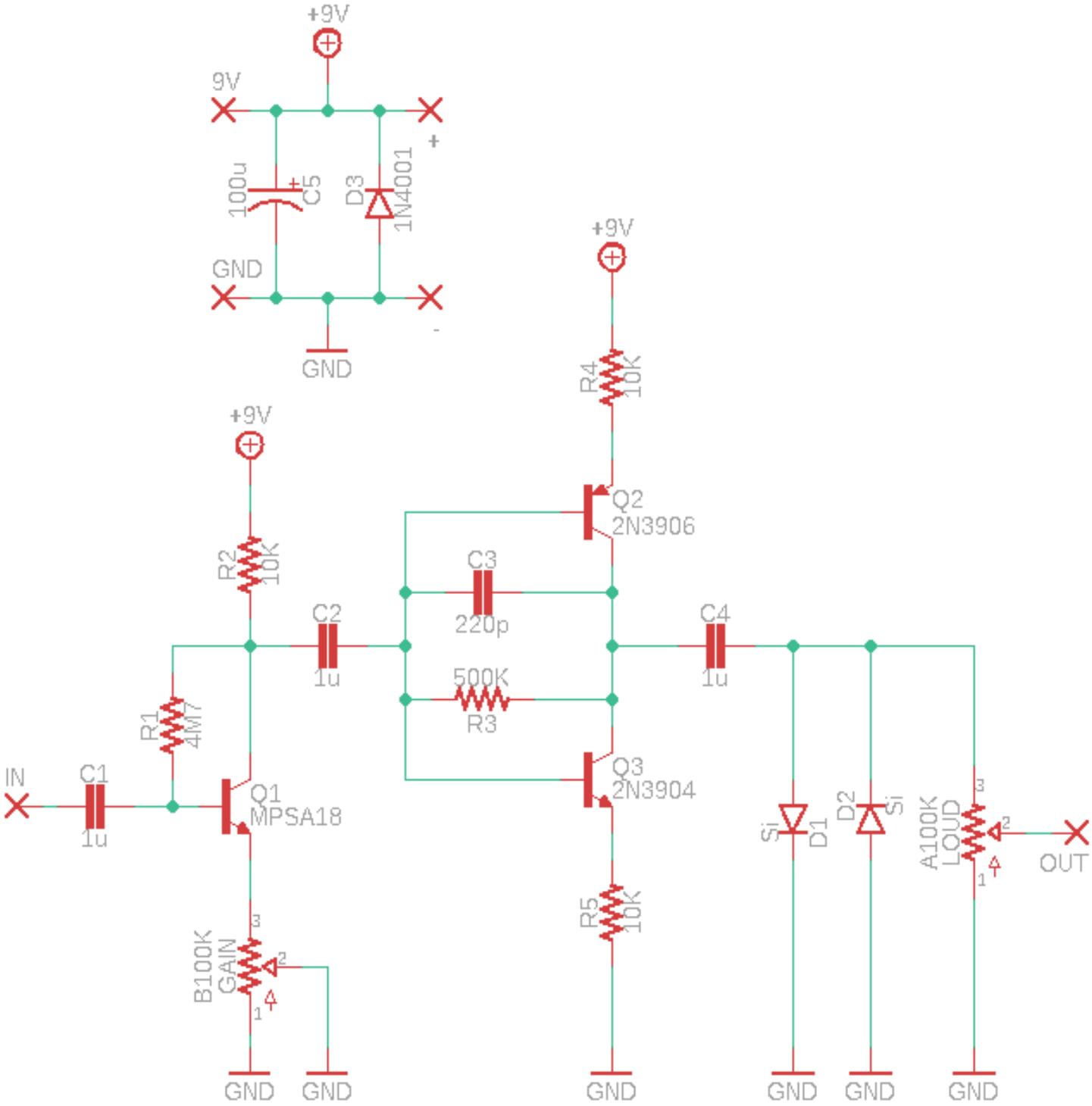
+9V
9V
+
100u
C5
D3
1N4001
GND
-
GND
+9V
R4
10K
Q2
2N3906
+9V
R2
10K
C3
220p
C2
1u
C4
1u
500K
R3
R1
4M7
IN
C1
1u
Q1
MPSA18
Q3
2N3904
Si
D1
D2
Si
A100K
LOUD
OUT
B100K
GAIN
R5
10K
GND
GND
GND
GND
GND
GND

Offboard Wiring